

- 5.72 Find V_o in the network in Fig. P5.72 using Thévenin's theorem.

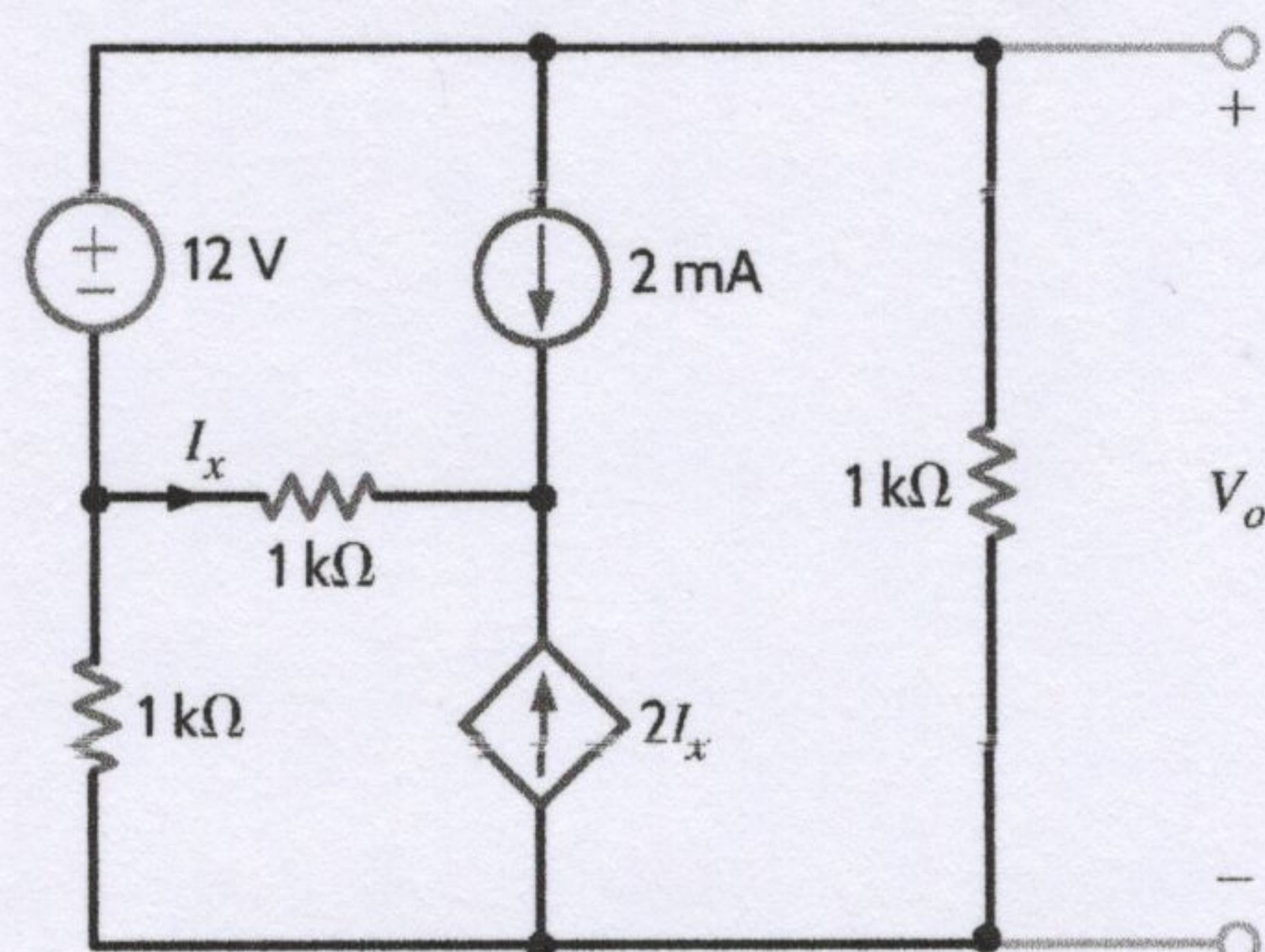


Figure P5.72

- 5.73 Find V_o in the network in Fig. P5.73 using Norton's theorem.

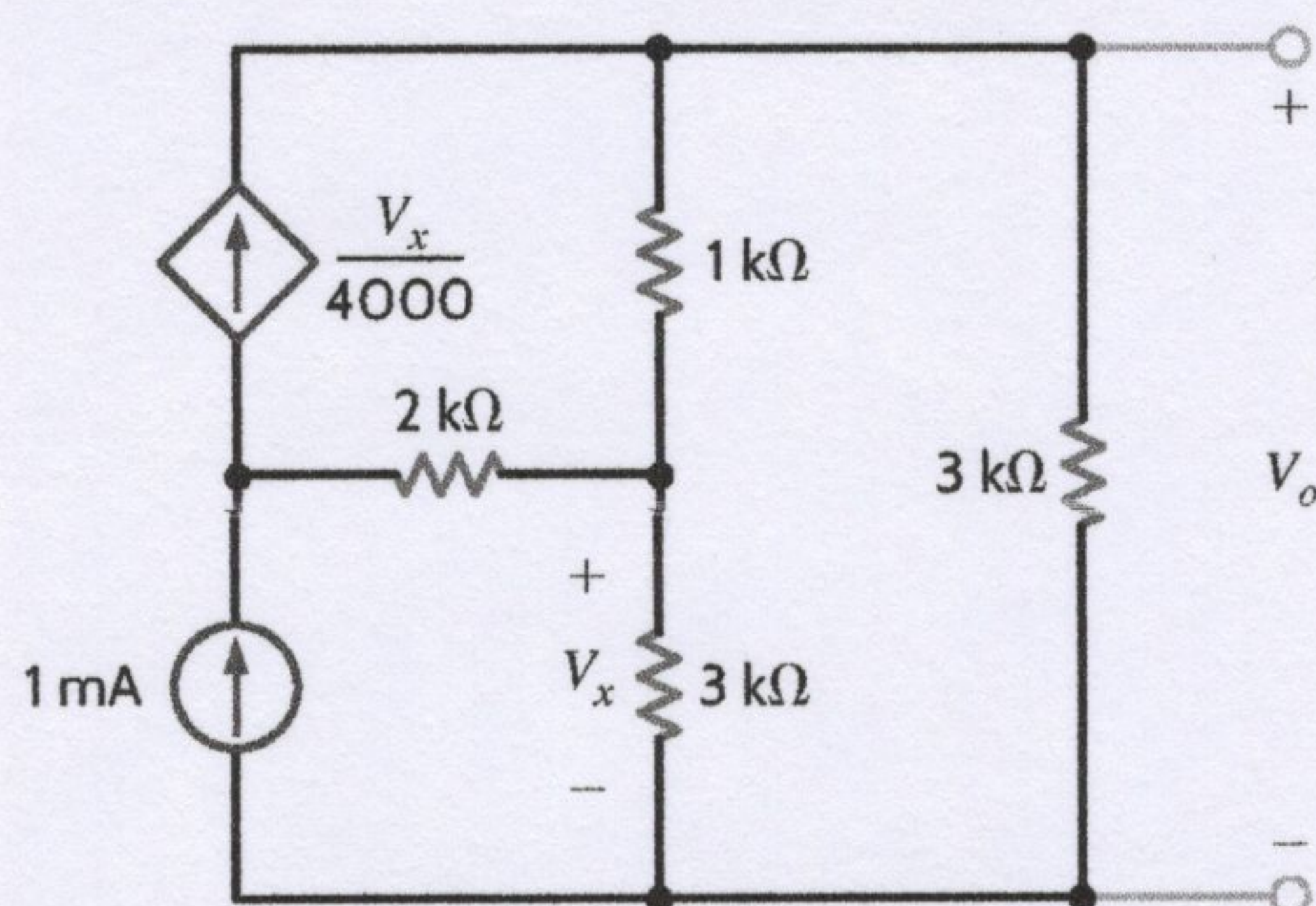


Figure P5.73

- 5.74 Use Thévenin's theorem to find the power supplied by the 2-V source in the circuit in Fig. P5.74.

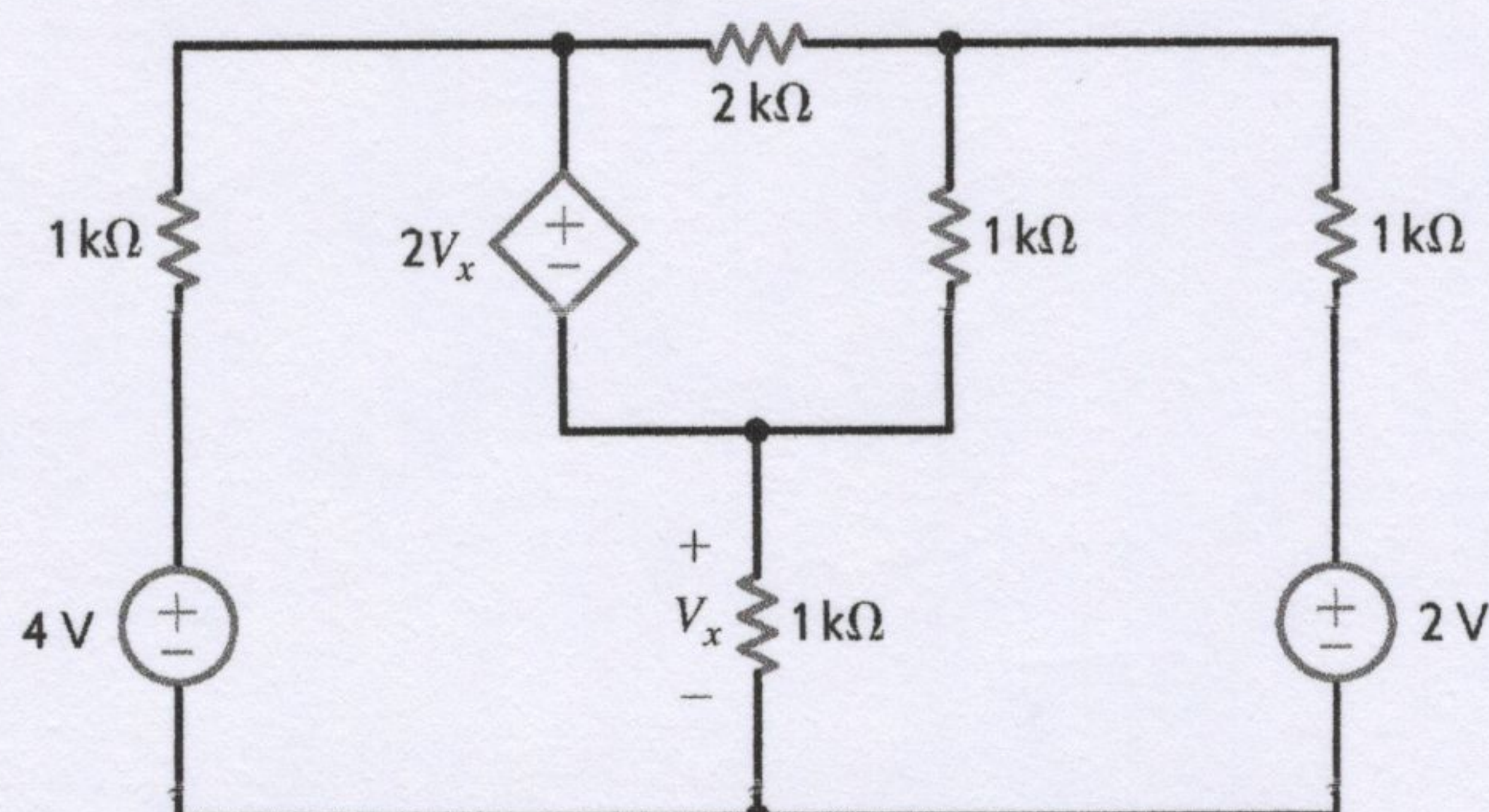


Figure P5.74

- 5.75 Find V_o in the circuit in Fig. P5.75 using Thévenin's theorem.

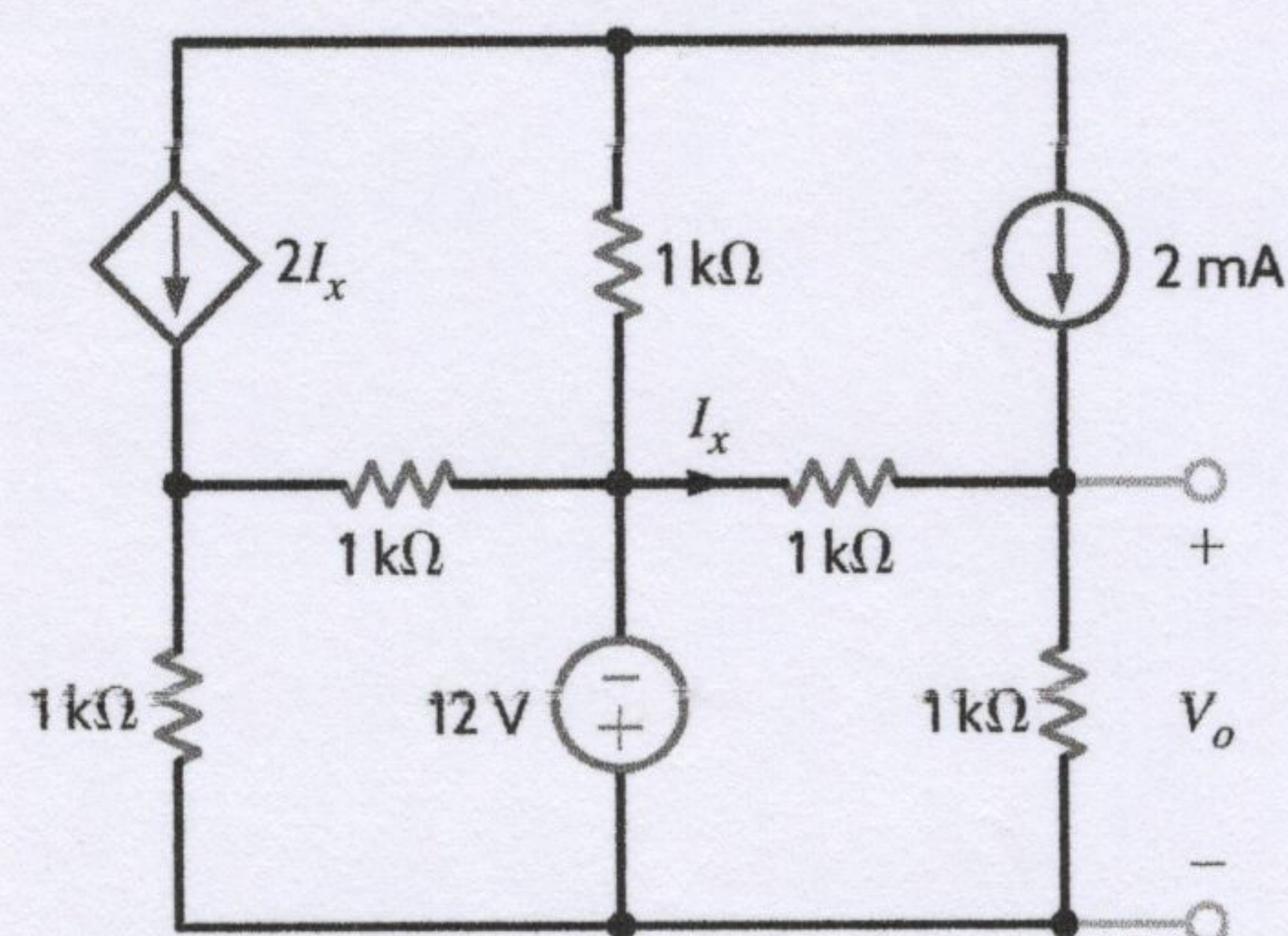


Figure P5.75

- 5.76 Find V_o in the network in Fig. P5.76 using Thévenin's theorem.

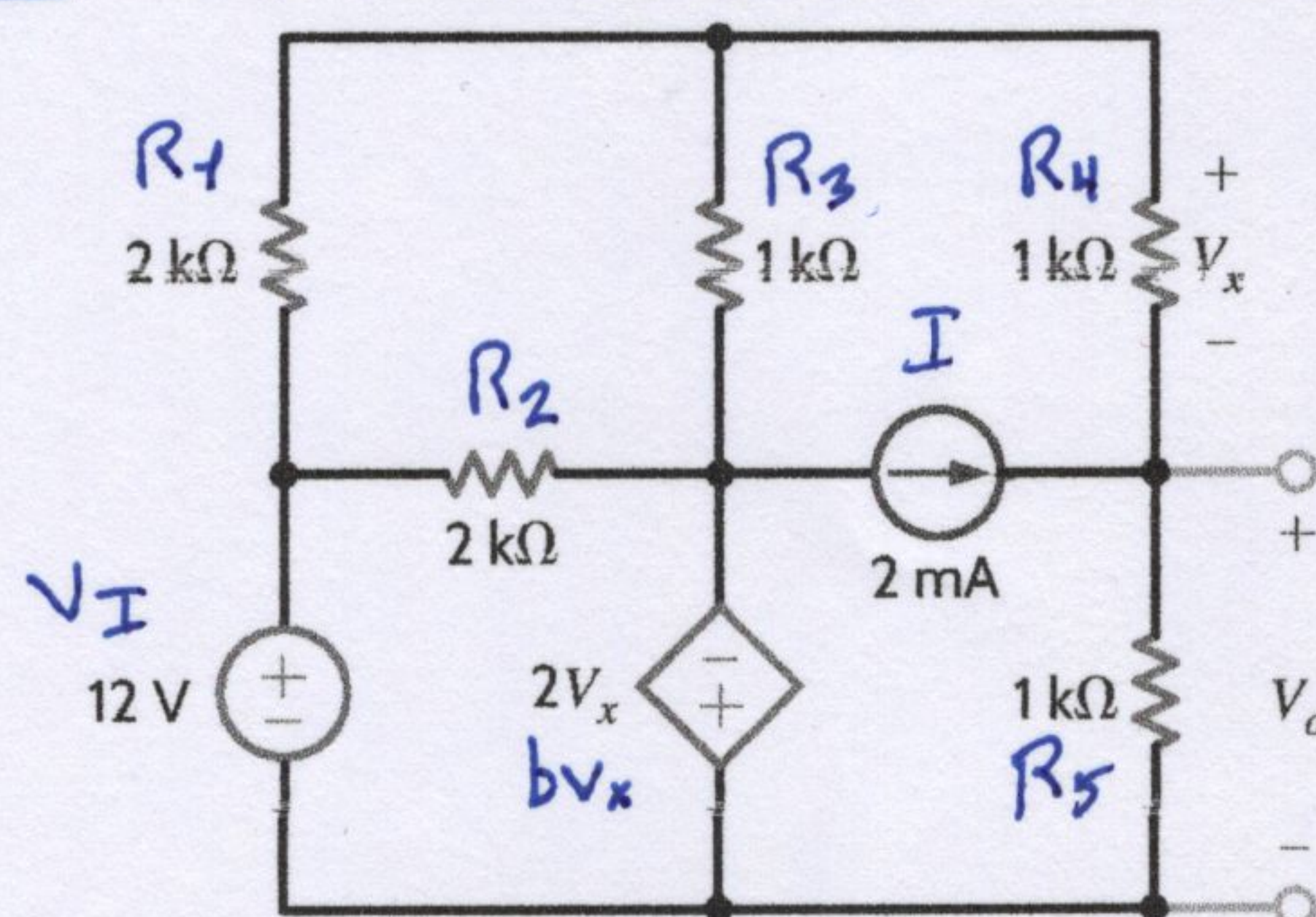


Figure P5.76

- 5.77 Find V_o in the network in Fig. P5.77 using Thévenin's theorem.

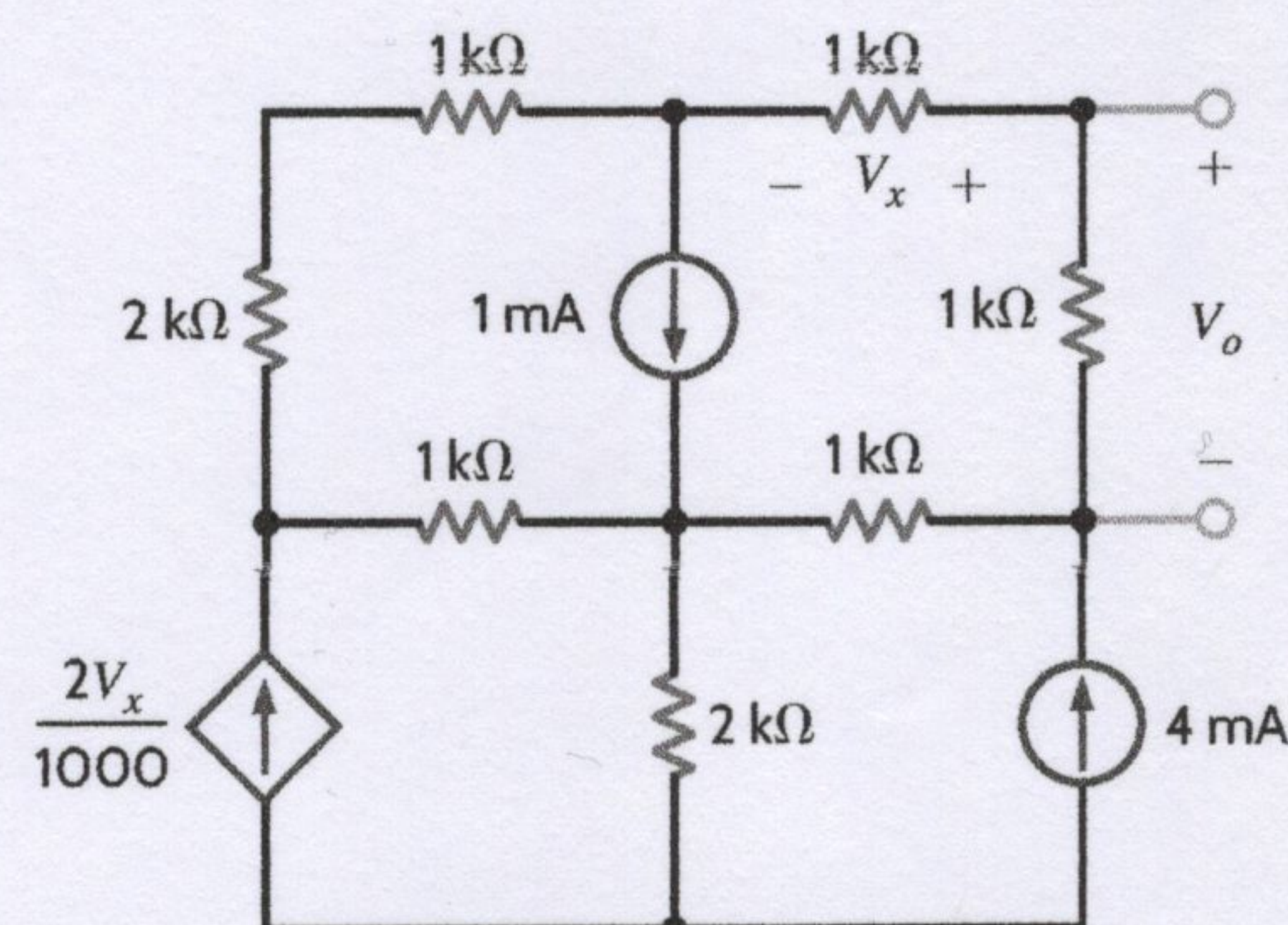


Figure P5.77

- 5.78 Use Thévenin's theorem to find I_2 in the circuit in Fig. P5.78.

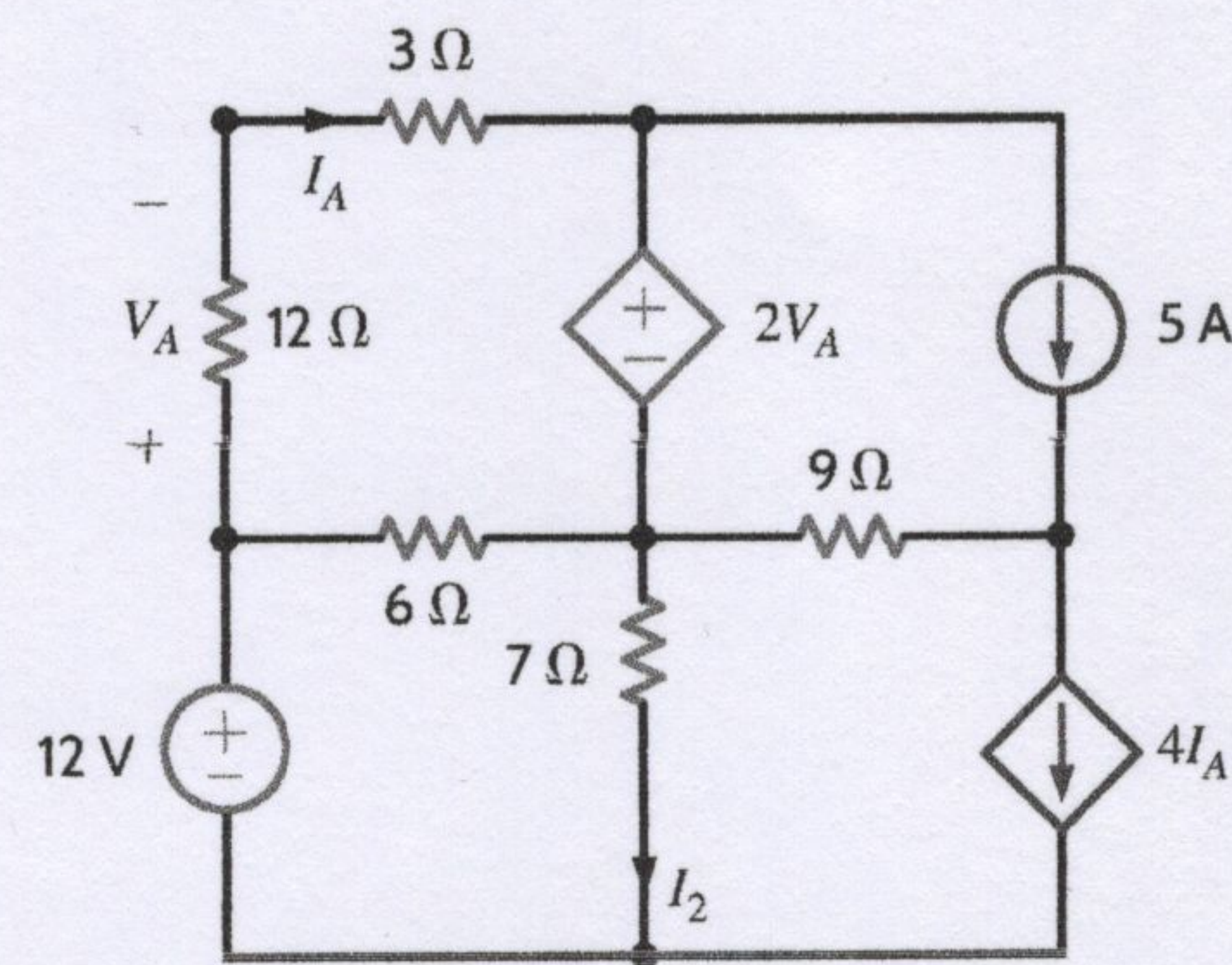


Figure P5.78

- 5.79 Use Thévenin's theorem to find V_o in the circuit in Fig. P5.79.


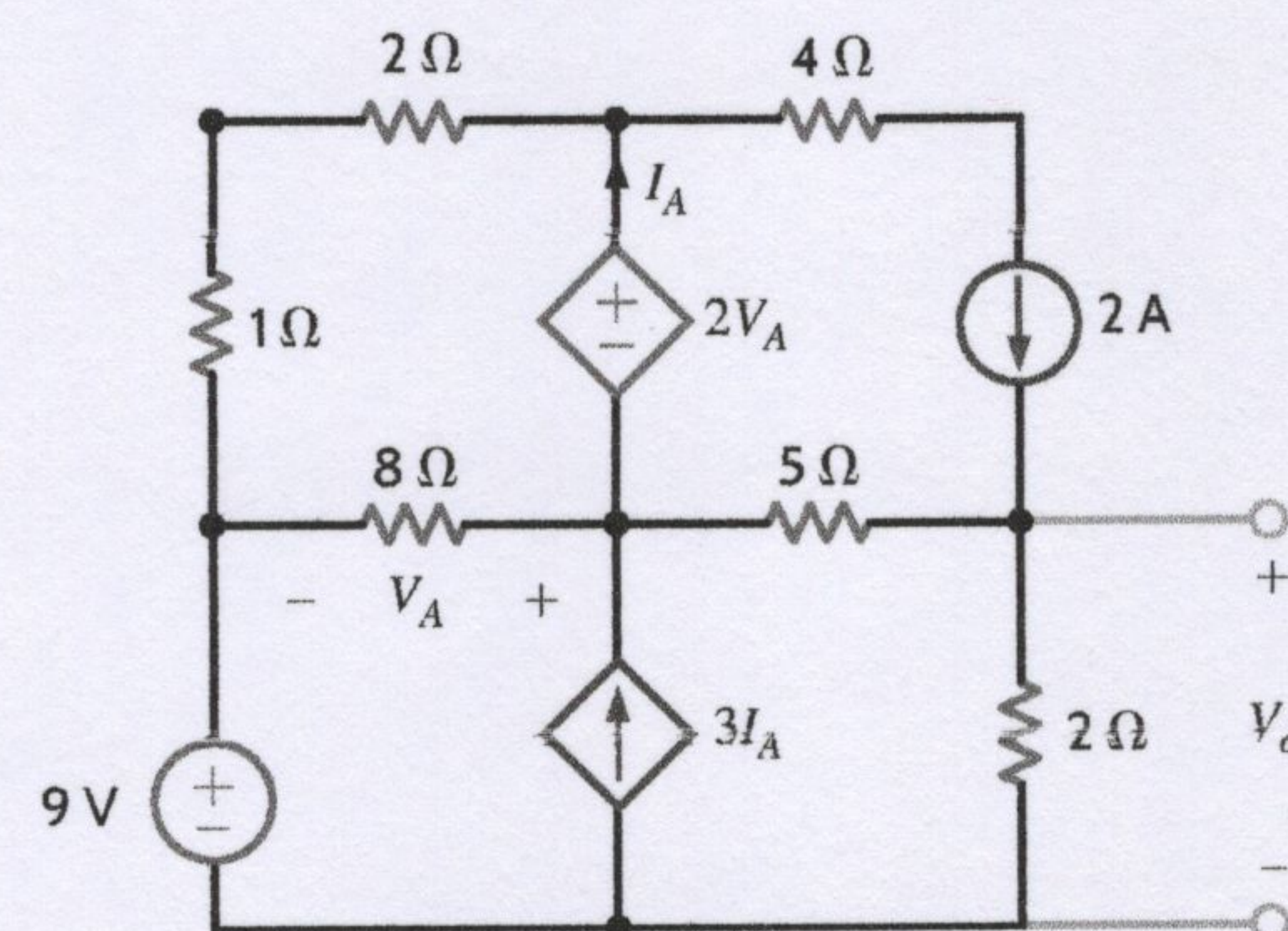


Figure P5.79

V_I alone.

Irwin & Nelms 11th ed,
problem 5.76 | Garek
Dyssel

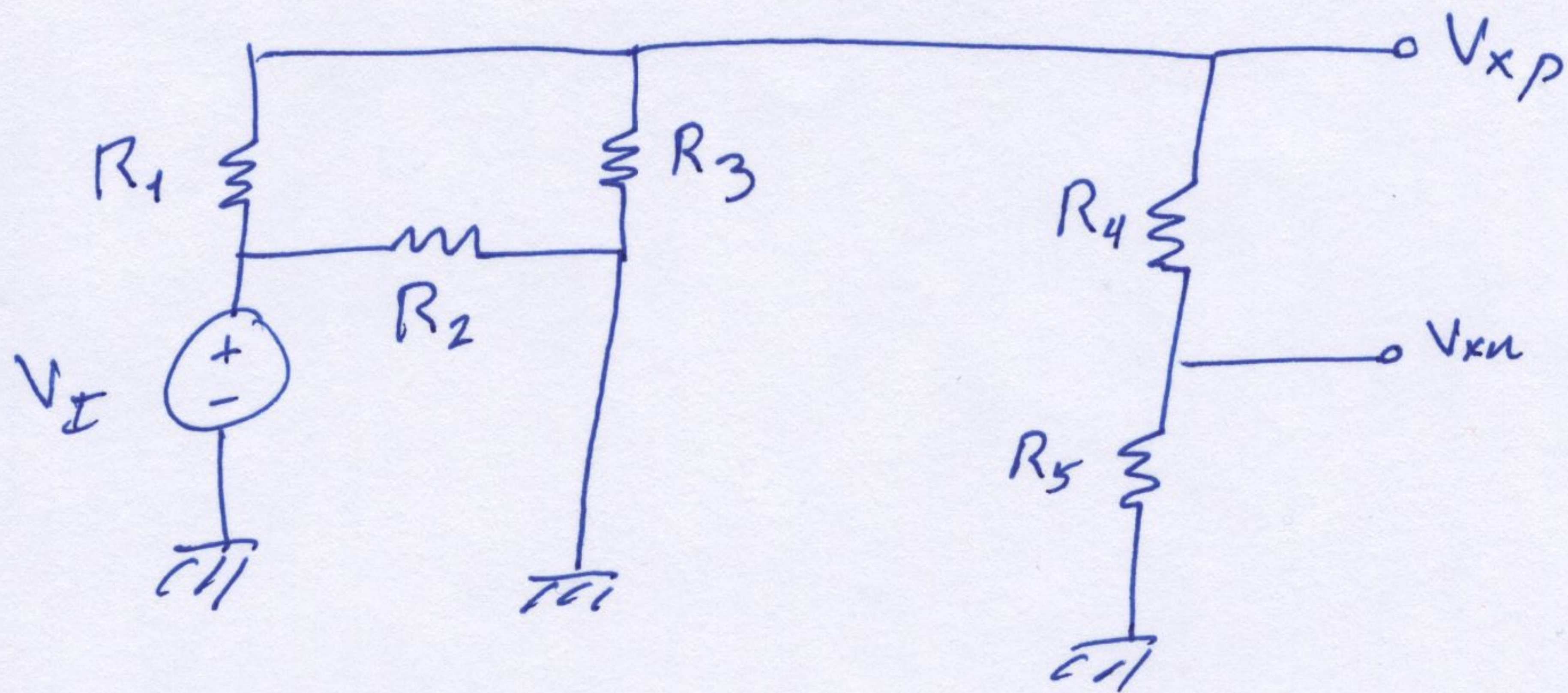



Inspection at node V_{xp} .

$$\frac{V_{xp}}{R_1 \parallel R_3 \parallel (R_4 + R_5)} = \frac{V_I}{R_1}$$

$$V_{xp} = \frac{V_I}{R_1} [R_1 \parallel R_3 \parallel (R_4 + R_5)]$$

$$V_{xn} = V_{xp} \frac{R_5}{R_4 + R_5}$$

bV_x alone

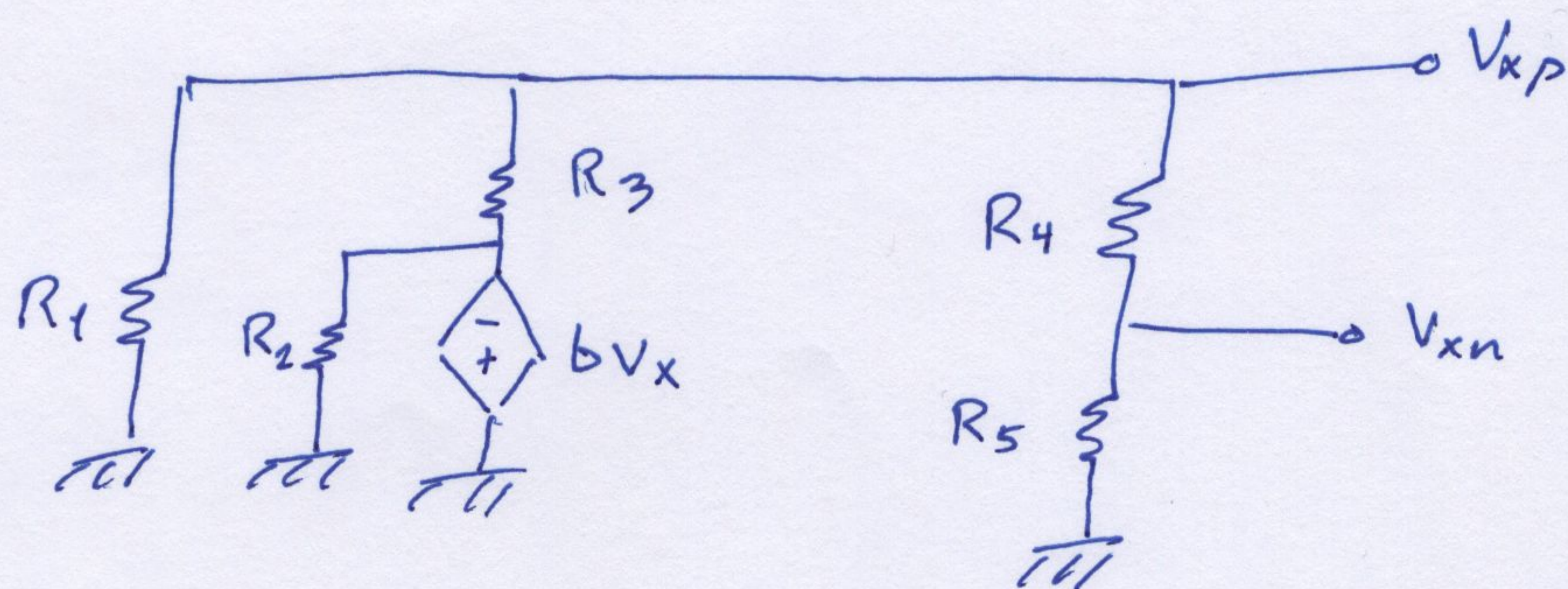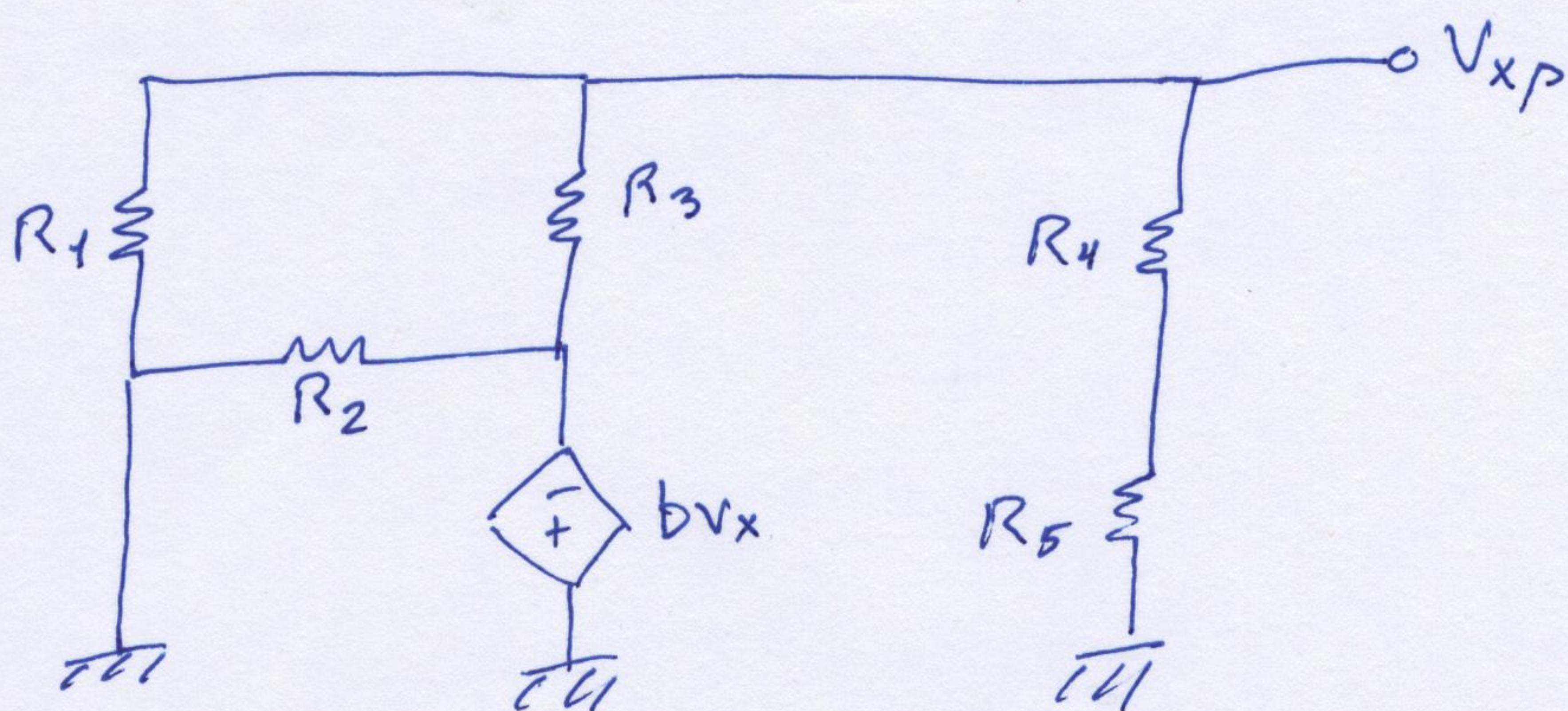



By inspection at node V_{xp} .

$$\frac{V_{xp}}{R_1 \parallel R_3 \parallel (R_4 + R_5)} = - \frac{bV_x}{R_3}$$

$$V_{xp} = - \frac{bV_x}{R_3} [R_1 \parallel R_3 \parallel (R_4 + R_5)]$$

$$V_{xn} = V_{xp} \frac{R_5}{R_4 + R_5}$$

I alone.

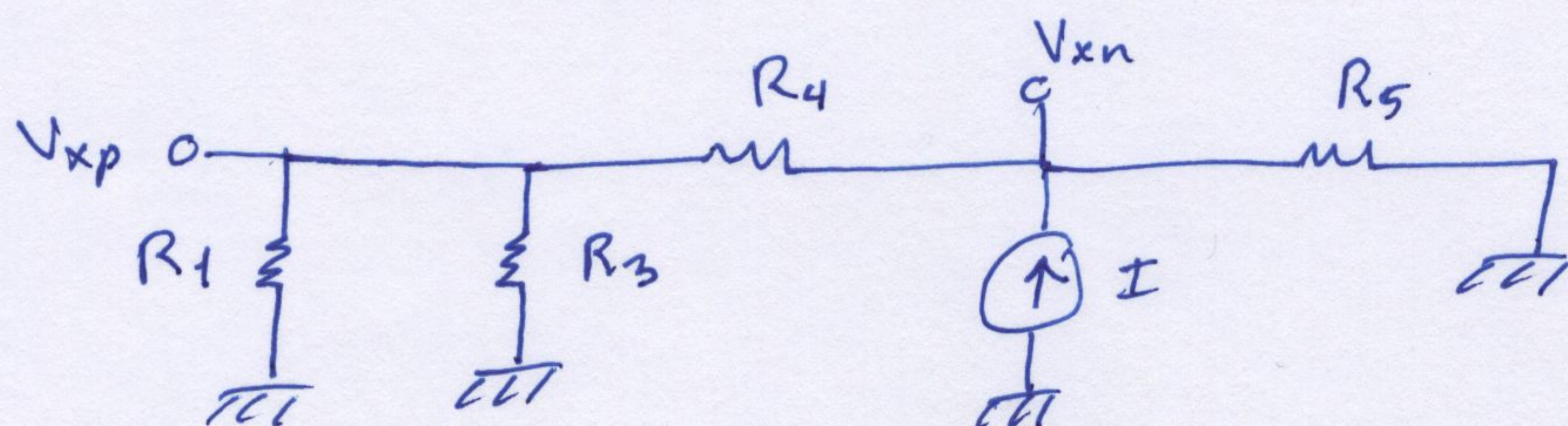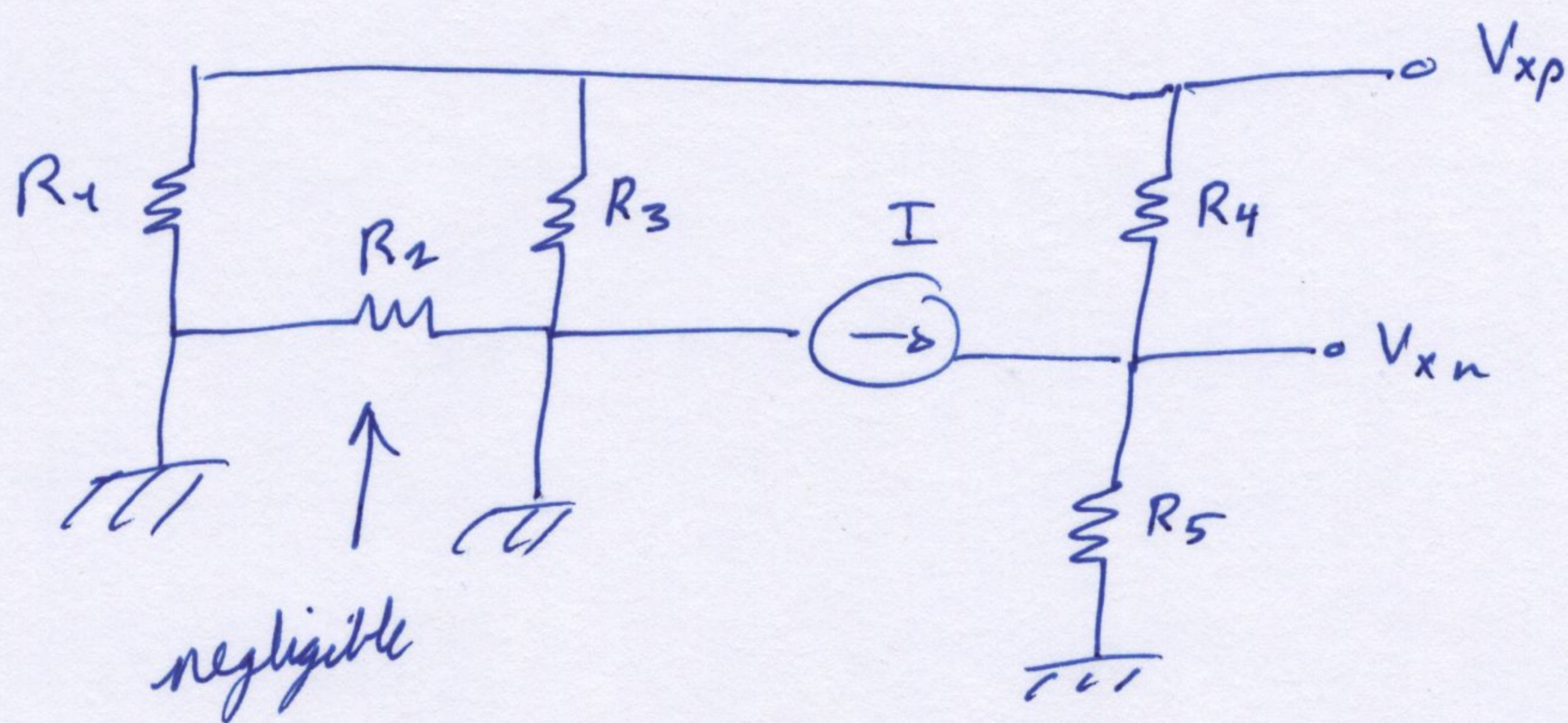

KCL @ node V_{xn} .

$$I = \frac{V_{xn}}{(R_1 || R_3) + R_4} + \frac{V_{xn}}{R_5}$$

$$I = \frac{V_{xn}}{[(R_1 || R_3) + R_4] || R_5}$$

$$V_{xn} = I [(R_1 || R_3) + R_4] || R_5$$

$$V_{xp} = V_{xn} \frac{(R_1 || R_3)}{(R_1 || R_3) + R_4}$$

V_{xp} for V_I alone

$$V_{xp1} = \frac{V_I}{R_1} [R_1 \parallel R_3 \parallel (R_4 + R_5)] \left(1 - \frac{R_5}{R_4 + R_5} \right)$$

V_{xp} for bV_x alone

$$V_{xp2} = - \frac{bV_x}{R_3} [R_1 \parallel R_3 \parallel (R_4 + R_5)] \left(1 - \frac{R_5}{R_4 + R_5} \right)$$

V_{xp} for I alone

$$V_{xp3} = I [(R_1 \parallel R_3) + R_4] \parallel R_5 \left(\frac{(R_1 \parallel R_3)}{(R_1 \parallel R_3) + R_4} - 1 \right)$$

Apply superposition now. Solve for V_{xp} .

$$V_{xp} = V_{xp1} + V_{xp2} + V_{xp3}$$

$$V_{xp} - V_{xp2} = V_{xp1} + V_{xp3}$$

$$V_{xp} \left(1 + \frac{b}{R_3} [R_1 \parallel R_3 \parallel (R_4 + R_5)] \left(1 - \frac{R_5}{R_4 + R_5} \right) \right) = V_{xp1} + V_{xp3}$$

~~$\frac{V_I}{R_1} [R_1 \parallel R_3 \parallel (R_4 + R_5)] \left(1 - \frac{R_5}{R_4 + R_5} \right)$~~


~~V_{xp1}~~

$$R_a = R_1 \parallel R_3 \parallel (R_4 + R_5)$$

$$R_b = [(R_1 \parallel R_3) + R_4] \parallel R_5$$

$$V_{xp} = \frac{\frac{V_I}{R_1} R_a \left(1 - \frac{R_5}{R_4 + R_5} \right) + I R_b \left[\frac{(R_1 \parallel R_3)}{(R_1 \parallel R_3) + R_4} - 1 \right]}{1 + \frac{b}{R_3} R_a \left(1 - \frac{R_5}{R_4 + R_5} \right)}$$

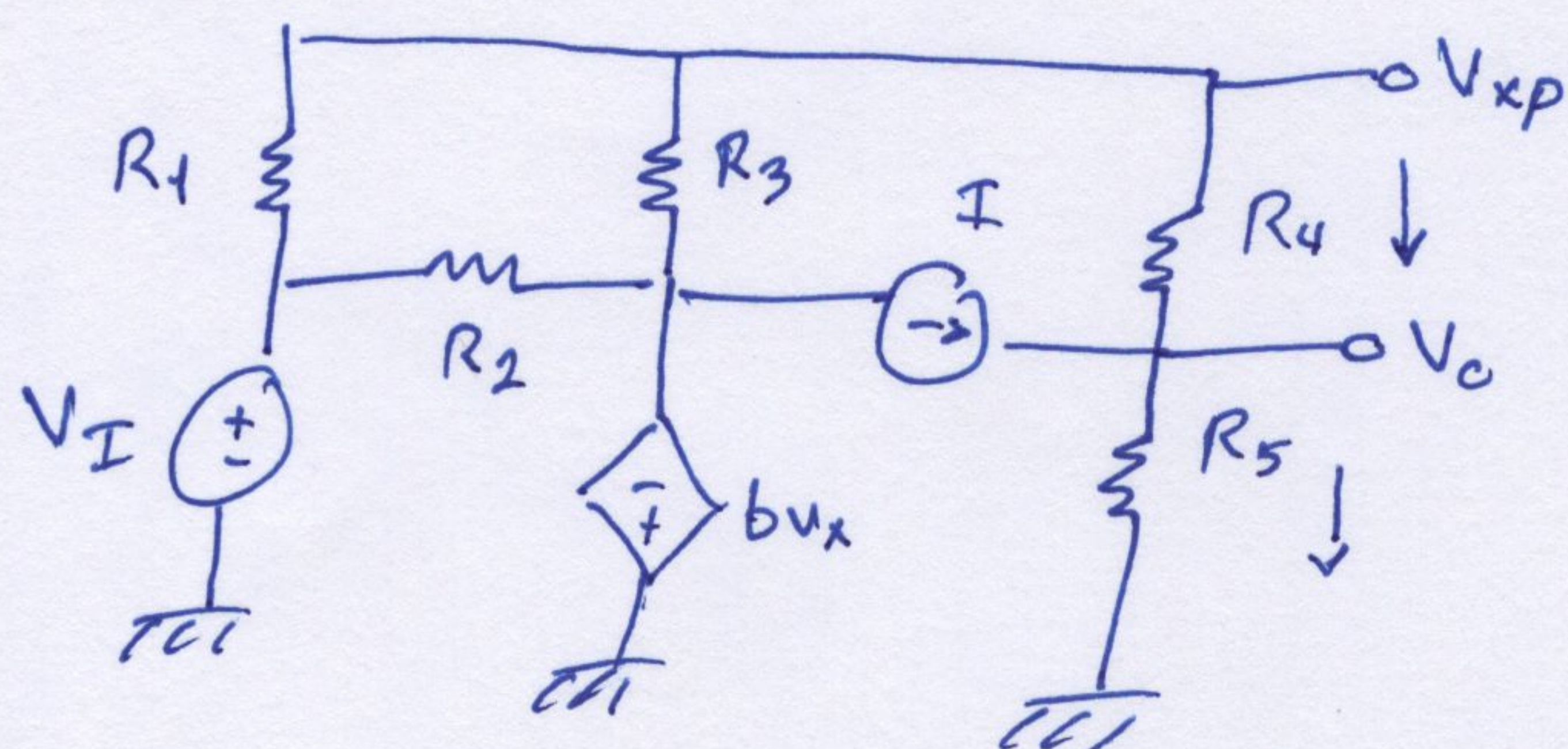Now back to the full circuit to find V_o .



$$\frac{V_{xp} - V_o}{R_4} + I = \frac{V_o}{R_5}$$

$$V_o = \left(\frac{V_{xp}}{R_4} + I \right) (R_4 \parallel R_5)$$

Calculate numerical values,

$$R_a = 2k \parallel 1k \parallel (1k + 1k) = 500 \Omega$$

$$R_b = [(2k \parallel 1k) + 1k] \parallel 1k = 625 \Omega$$

$$V_{xp} = \frac{\frac{12V}{2k} (500) \left(1 - \frac{1}{2}(1k)\right) + (2mA)(625) \left(\frac{666.67}{666.67 + 1k} - 1\right)}{1 + \frac{2}{1k} (500) \left(1 - \frac{1}{2}(1k)\right)}$$

$$\boxed{V_{xp} = 3.00753V}$$

$$V_o = \left(\frac{3.00753V}{1k} + 2mA \right) \left(\frac{1}{2}(1k) \right)$$

$$\boxed{V_o = 2.5038V}$$